

## HOMEWORK 2

Name: Matthew Galitz


Computing ID: ykkbrh

Collaborators: NONE!

**Collaboration Policy: For this homework only!** You may collaborate with other students in this class. As an **exception** to the usual collaboration policy, you do not need to tell us about casual interactions of the "I got X, what did you get?" variety. But **do** cite any close collaboration or major corrections; for example if the answer to the above hypothetical was "I think X is wrong, here's why" and then you change your answer, add a note like "mst3k suggested this answer" next to your answer. However, we expect that everyone will work on the assignment to better understand circuits, so **you may not directly copy another student's answer.**

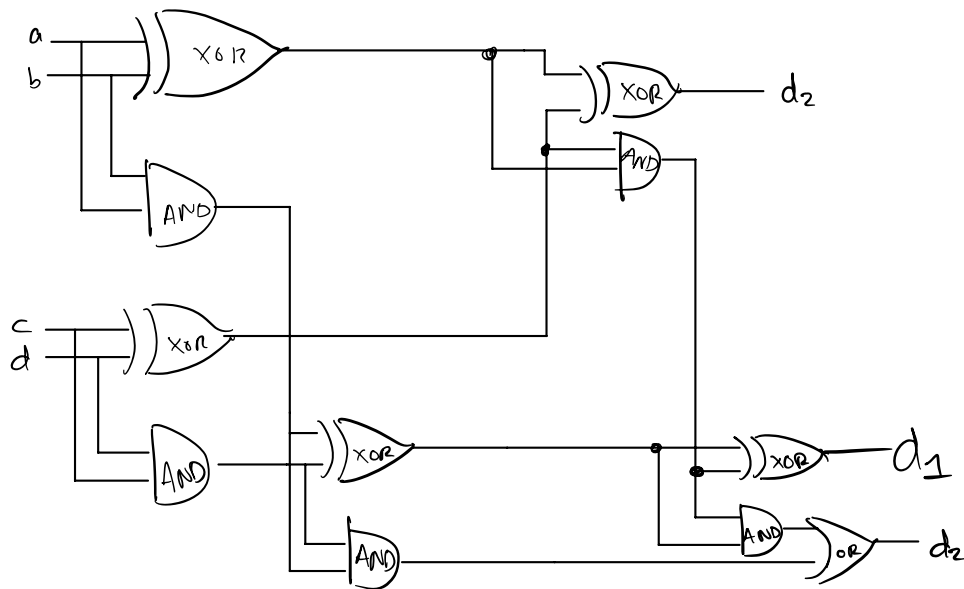
### PROBLEM 1 4-input adder

We have discussed both a 2-input and 3-input adders for single-bit values as we were building our ripple carry adder. Draw a 4-input adder for single-bit values: that is, a set of logic gates with 4 input wires (no need to name them) each representing a number between 0 and 1 and a multi-bit output  $z$ , composed of wires  $z_0$  through  $z_n$  (where  $z_0$  is the low-order bit,  $z_1$  the next, etc., up to the number of wires needed for this task). The gates should ensure that  $z =$  the sum of all four inputs.


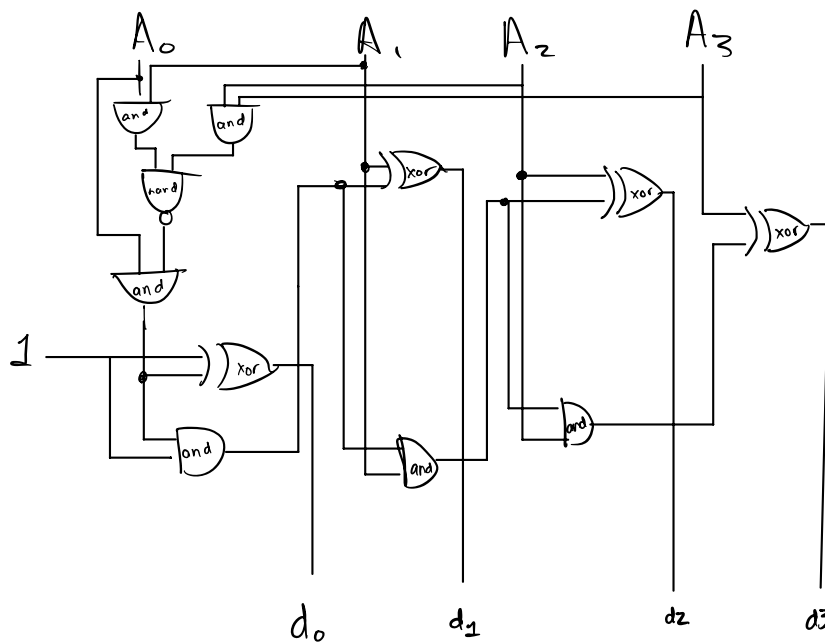
## PROBLEM 2 4-bit increment to 15

In class we considered an increment circuit that adds 1 to its input value. How can we change our circuit to “stop” at  $x = 0b1111$ ? That is, if  $x$  is not all 1s, then increment by 1. If  $x$  is all 1s, then increment by 0, i.e.,  $z = 0b1111$ . Draw a circuit that does not use more than twice the number of gates in the original.




0 → least significant



3 → most significant

the output  
should be  
reflected

## PROBLEM 3 4-bit decrement

Now, rather than our 4-bit increment circuit that adds 1 to its input value, we want a circuit that subtracts 1 (i.e.,  $z = x - 1$ ). Draw a 4-bit decrement circuit that does **not** use not ( $\sim$ ) gates.

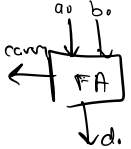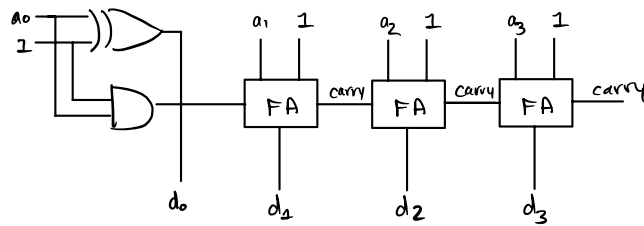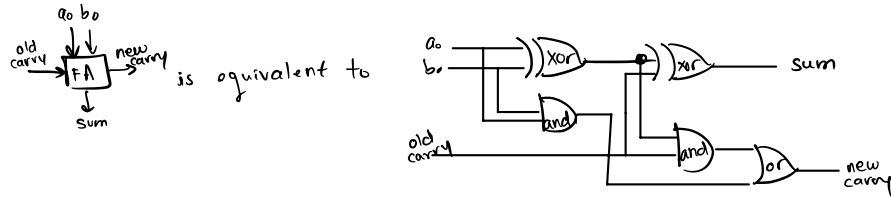I will use  as shorthand for a full-adder.



PROBLEM 4 *Fancy adder*

Given two 4-bit inputs  $x$  and  $y$ , draw a circuit that output the value  $z$  such that  $z = x + x + y$ . As a special property of **this circuit only**, we do **not** want overflow, so we have decided that  $z$  may have more than 4 bits to represent its value. Draw the corresponding circuit; label the output bits of  $z$  and state the number of bits needed in the output. *Hint: is there a fast way to calculate  $x + x$  without using many gates?*

